


- Digital Logic

- Turing Machine

① Arith $+ \equiv (-, \times, \div)$

② $+ \equiv \text{AND}, \dots$

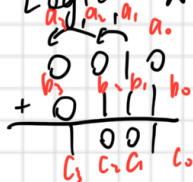③ Logical And / OR / NOT can do everything




$$c_0 = a_0 + b_0 \equiv a_0 \text{ XOR } b_0$$




$$c_1 = a_1 + b_1 \equiv a_1 \text{ XOR } b_1$$

$$\text{Carry}_1 = a_1 \text{ AND } b_1$$


exclusive OR

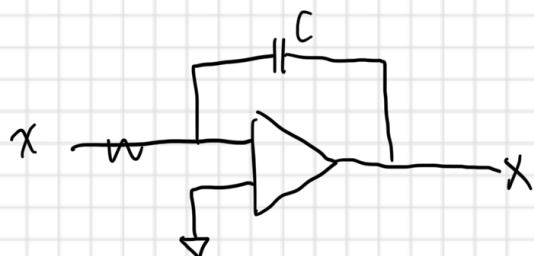

Logic: AND, OR, NOT

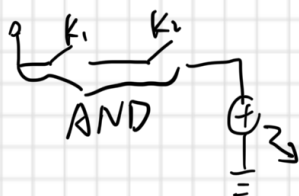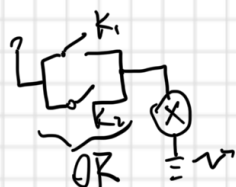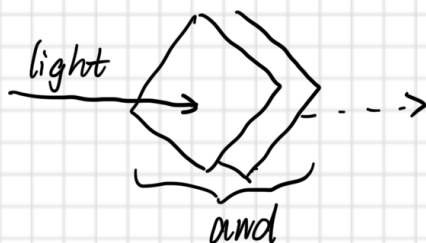





Relay

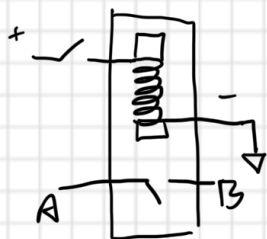

① $Y = A \cdot B$ (AND)

② $Y = A + B$ (OR)

③ $Y = \bar{A}$

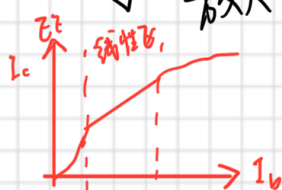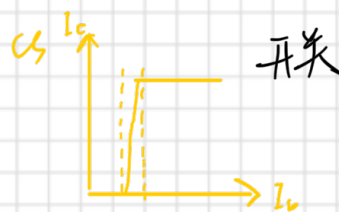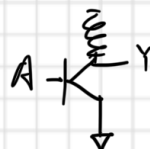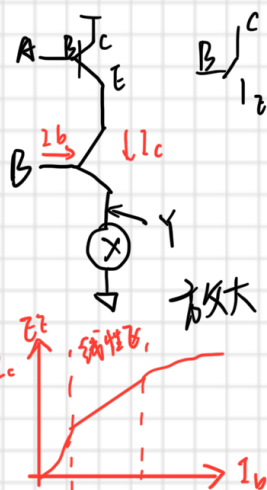


Mem Tech

Combination logic vs stateful logic


AND ...

Volatile (C)

Volatile int X;
 size ← unig. address

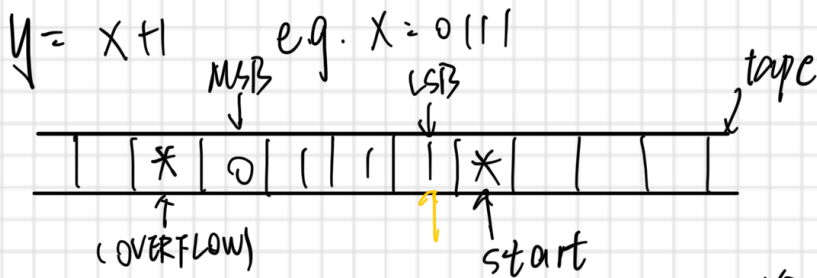
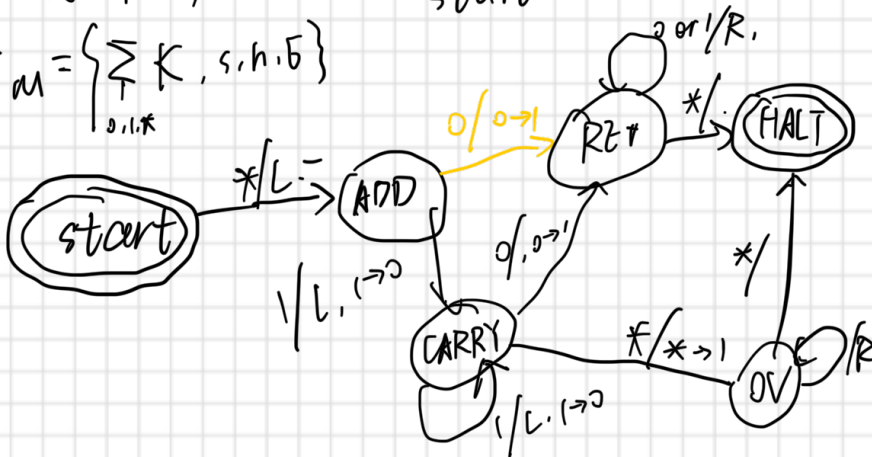
$$T_m = \left\{ \sum_{0,1,*} K, s, h, b \right\}$$



Cur State	input	$\begin{matrix} x \rightarrow 0/1 \\ 0 \rightarrow 1 \\ 1 \rightarrow 0 \\ 0,1 \rightarrow * \end{matrix}$ write	$\begin{matrix} L-R \text{ or } \dots \\ \text{shift} \end{matrix}$
ADD	$\begin{matrix} 0 \\ 1 \\ 2 \end{matrix}$		
RET			
CARRY			
OV			